
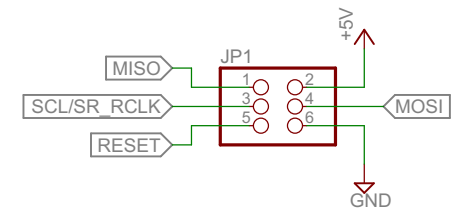
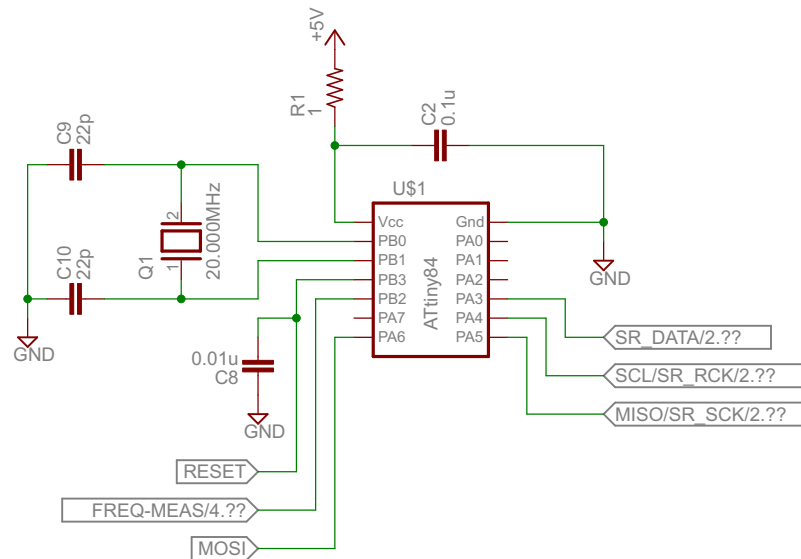



Ryan Jensen


2016-April



FreqCount84

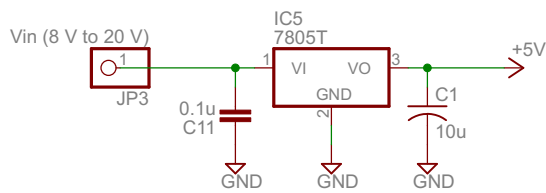A frequency counter designed around the ATtiny84



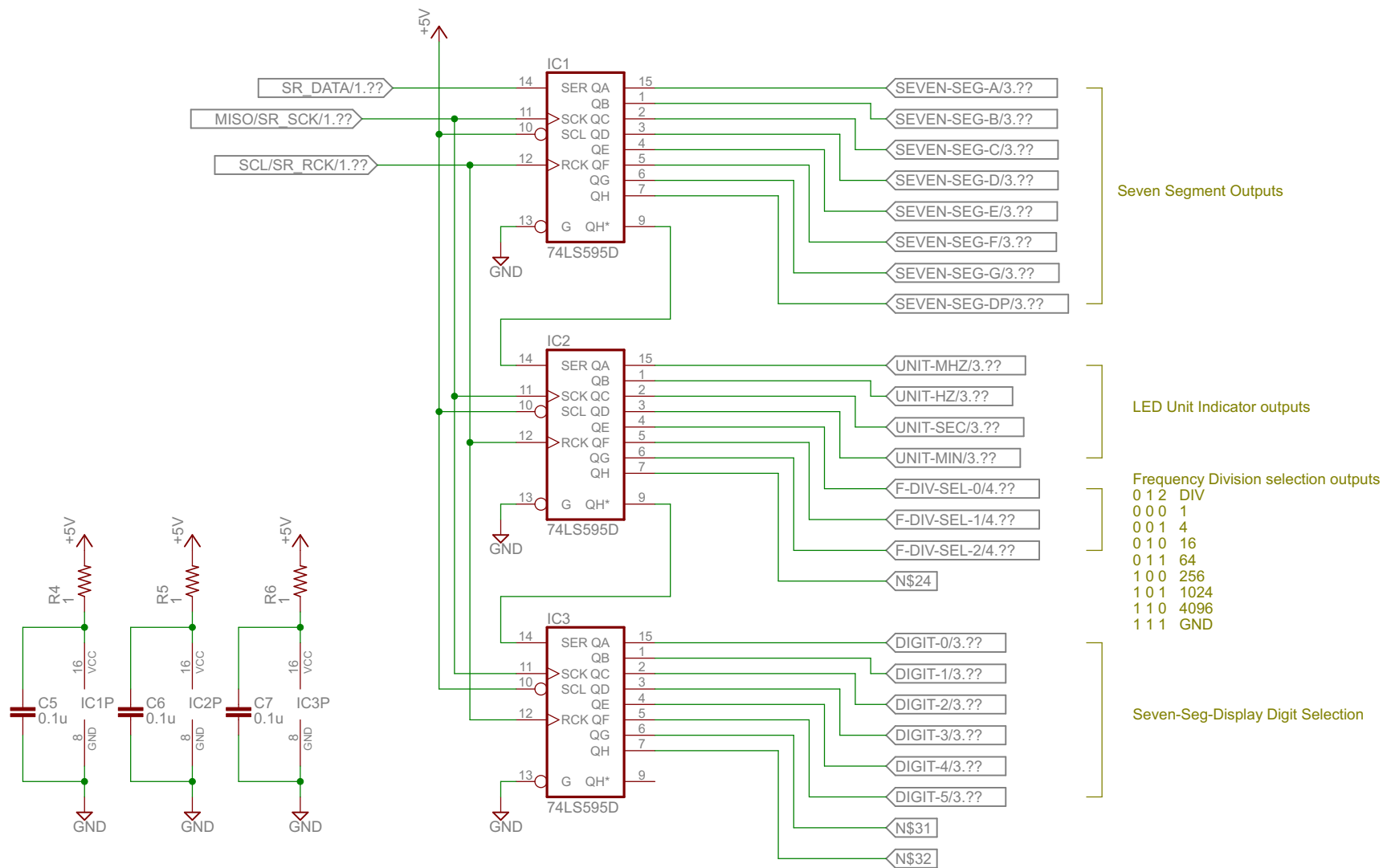

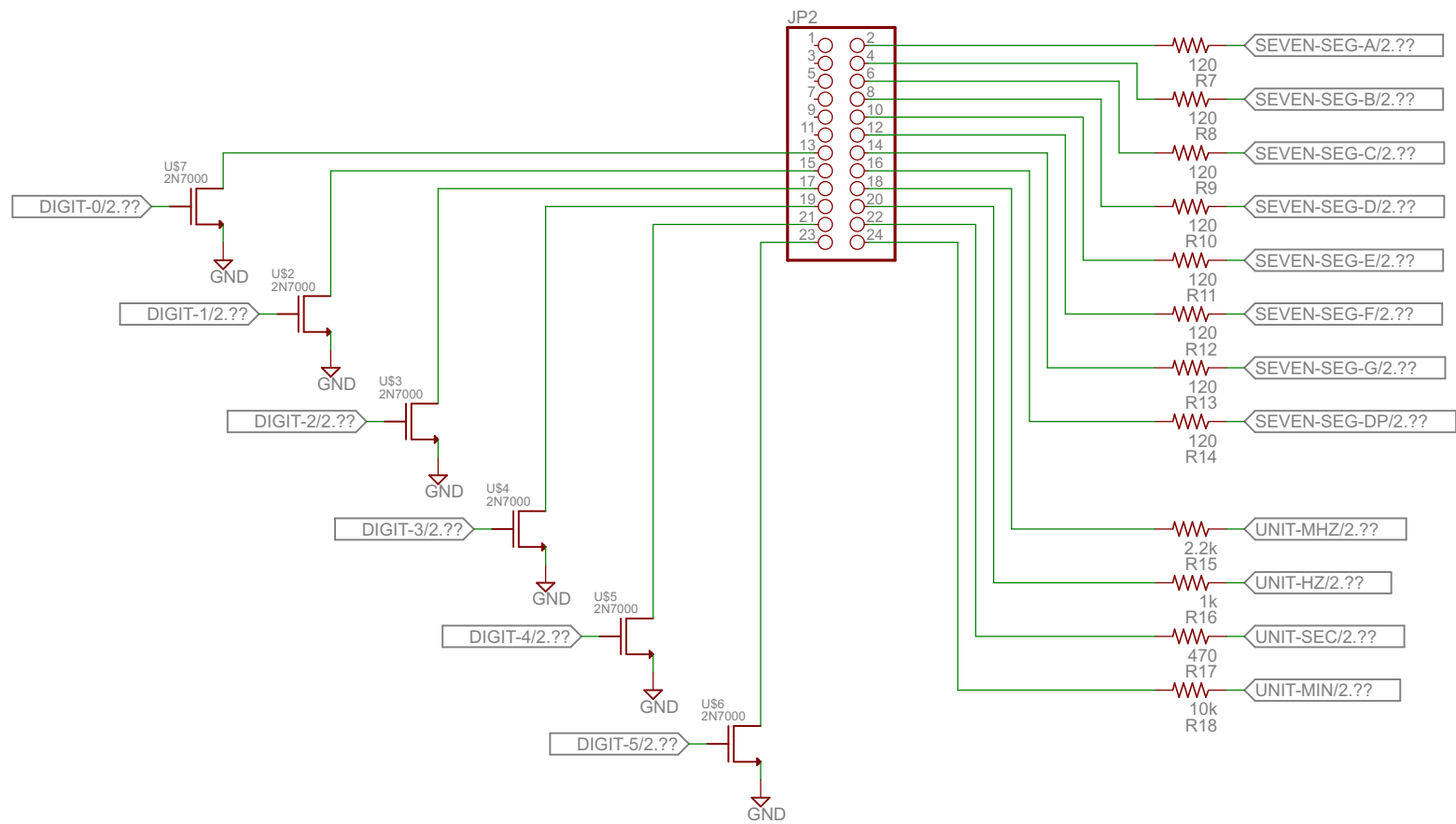

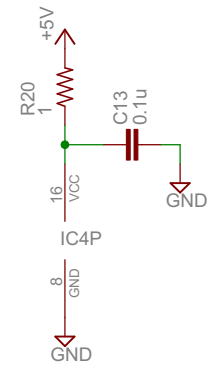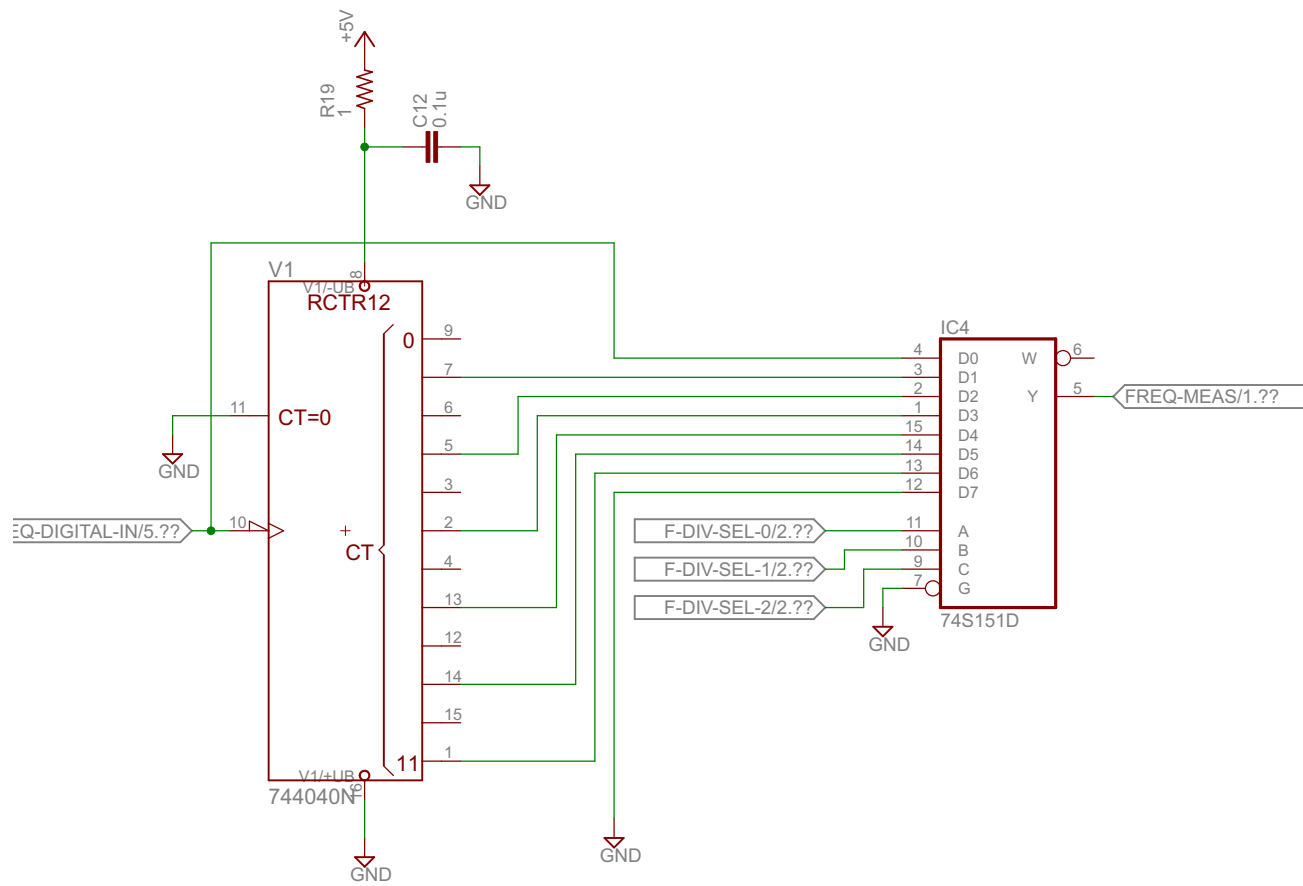

Switch Position 1: AC Coupling

This signal path will amplify and digitize the signal (clip the signal to 0 or 5 V).


This is intended to work for high frequency signals.

The input impedance should be around 91 k Ω for frequencies where the reactance of the input cap and the logic gate's capacitance are negligible.

The lower bound is determined by the time of the input AC-coupling filter (time constant = $C4 * R3 || R21$). The high frequency bound is determined by the RC lowpass filters. This is probably something up in the 10's of MHz.

I am relying on the input capacitance of the inverters and the 470 ohm resistors to filter the signal to prevent the inverters from oscillating.

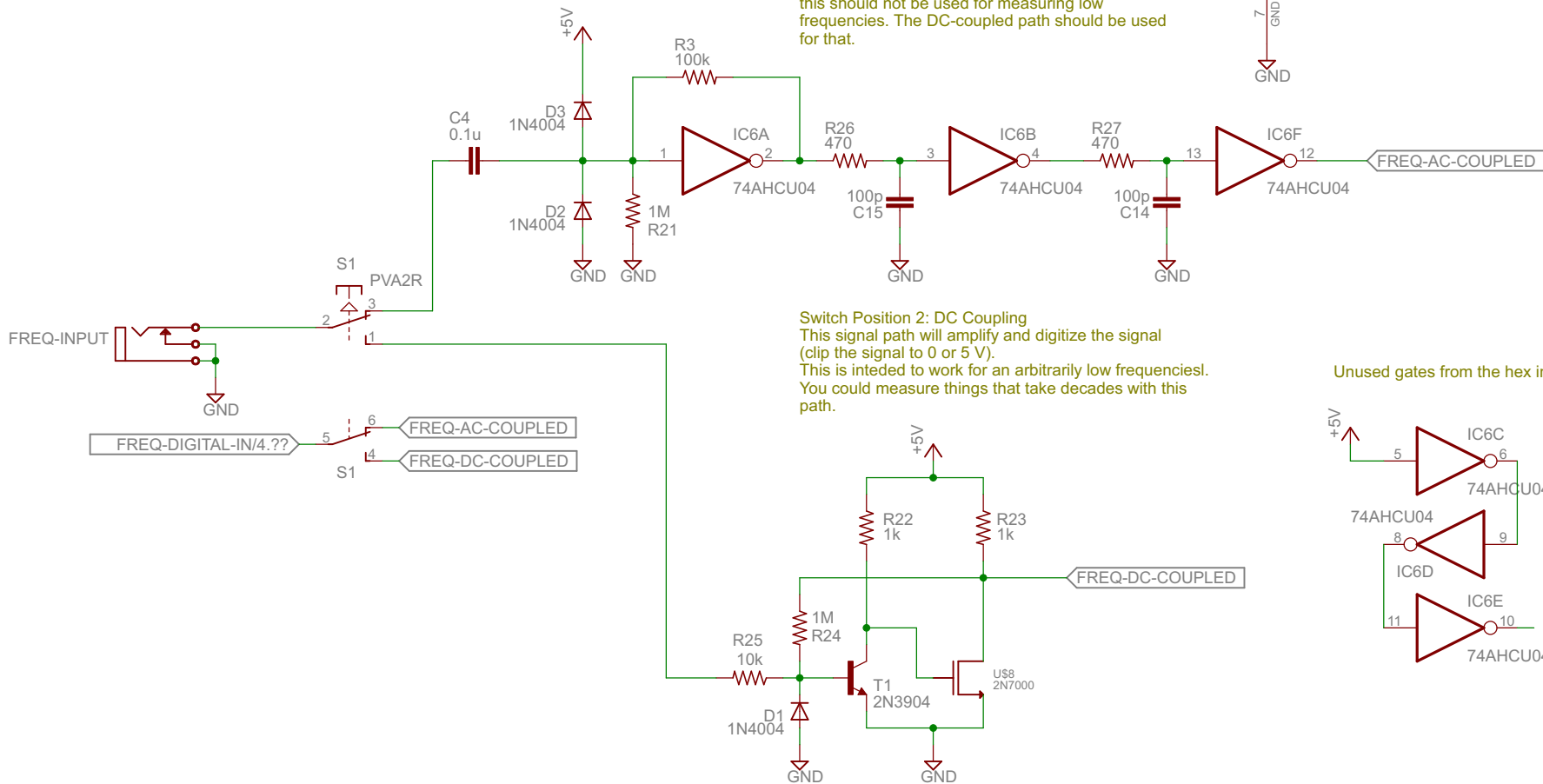As per the datasheet, the input capacitance is 10 pF. Experimentally, I found that this stage oscillates on transitions when the transition is slow. Hence, this should not be used for measuring low frequencies. The DC-coupled path should be used for that.



Switch Position 2: DC Coupling

This signal path will amplify and digitize the signal (clip the signal to 0 or 5 V).

This is intended to work for an arbitrarily low frequencies!. You could measure things that take decades with this path.

Unused gates from the hex inverter chip

